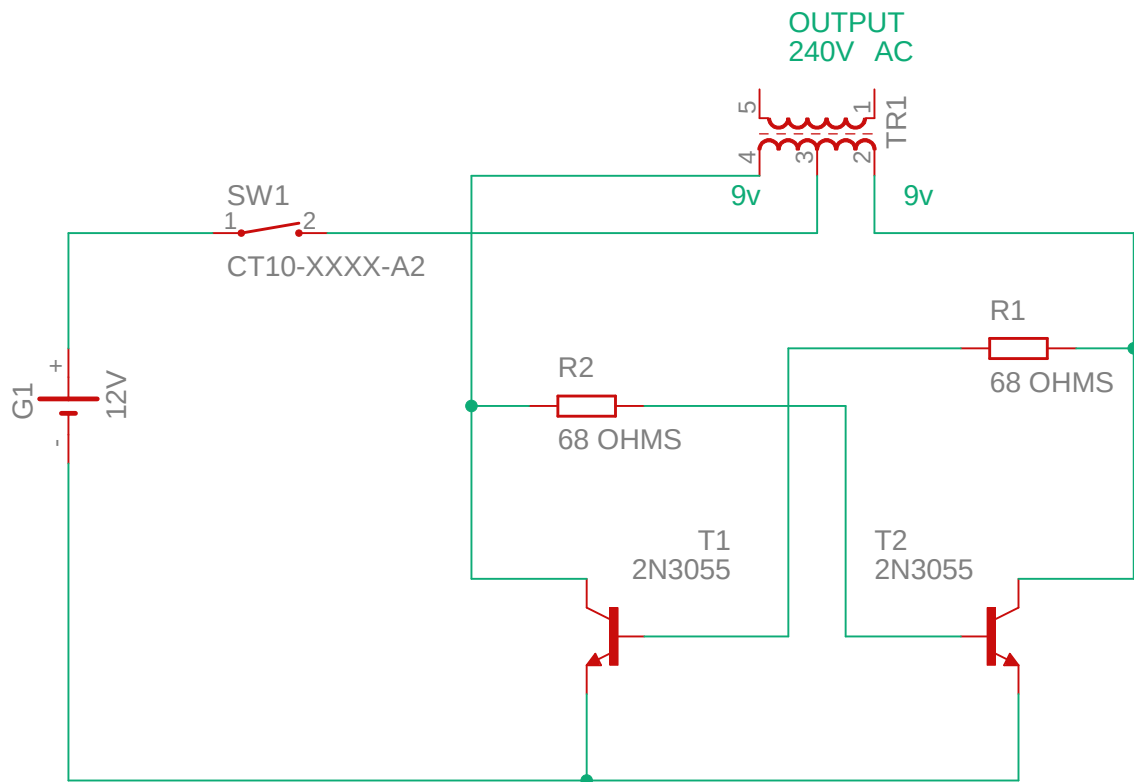


## ELECTRONICS PROJECT: SIMPLE INVERTER



SIMPLE INVERTER CIRCUIT:

INPUT 12VDC

OUTPUT 240V AC